

# Transconductance Amplifier


Shih-Chii Liu

Fall 2021


## Outline:

- Differential pair
- Transconductance amplifier (and its  $g_m$  and  $A$ )
- Voltage amplifier
- Wide range transconductance amplifier

# Differential Pair (I)

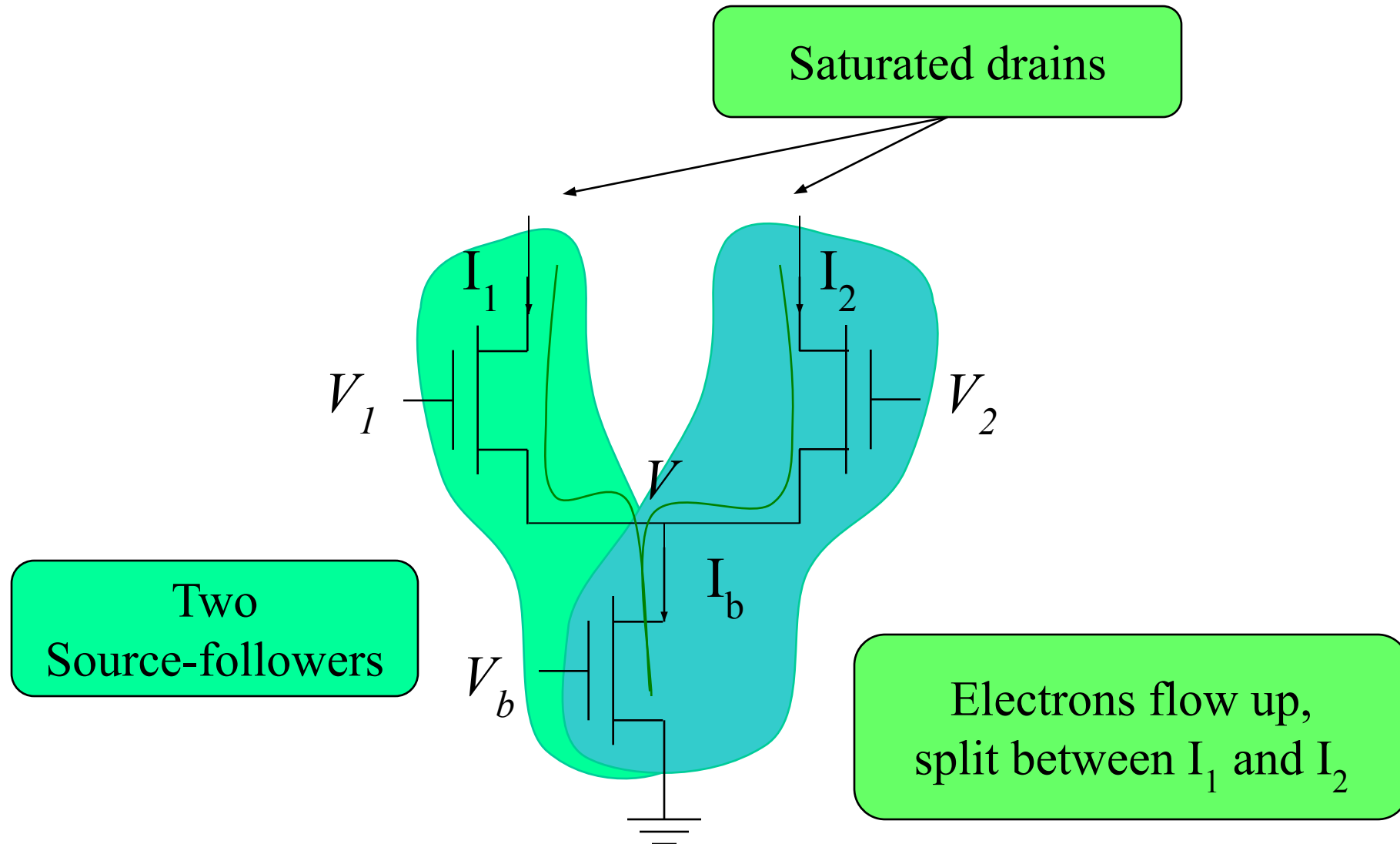

# Differential Pair (II)

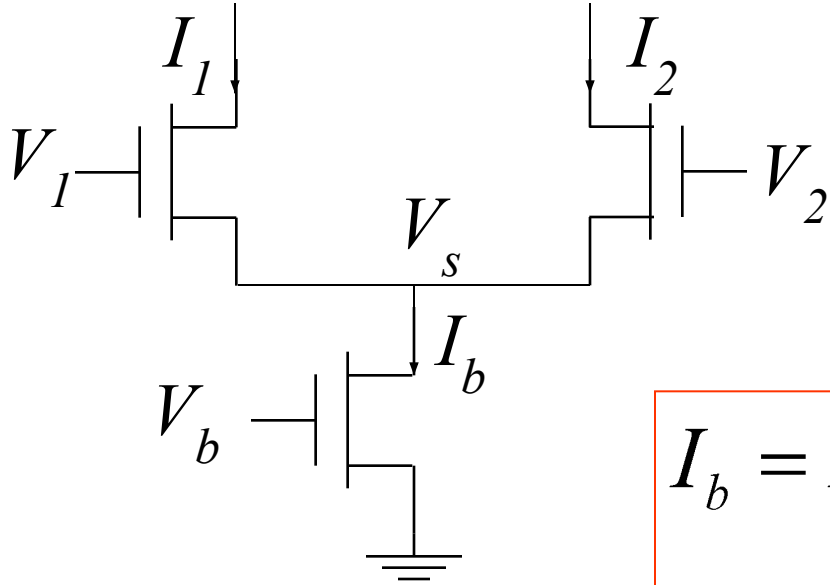


$$I_1 = I_0 e^{\kappa V_1 - V_s / U_T}$$
$$I_2 = I_0 e^{\kappa V_2 - V_s / U_T}$$

$$I_b = I_0 e^{\kappa V_b / U_T} = I_1 + I_2$$
$$= I_0 e^{-V_s / U_T} \left( e^{\kappa V_1 / U_T} + e^{\kappa V_2 / U_T} \right)$$

$$\Rightarrow e^{V_s / U_T} = \frac{e^{\kappa V_1 / U_T} + e^{\kappa V_2 / U_T}}{e^{\kappa V_b / U_T}}$$

# Differential Pair (II)

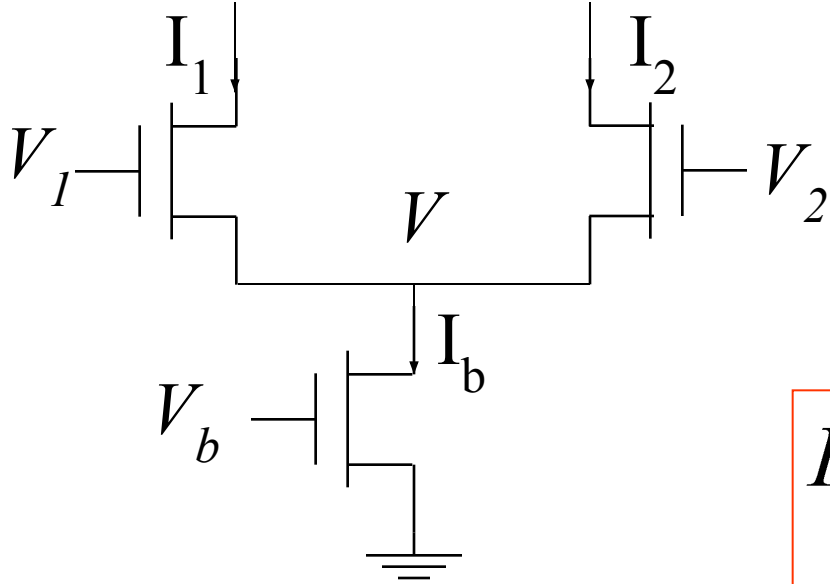


$$I_1 = I_0 e^{\kappa V_1 - V}$$

$$I_2 = I_0 e^{\kappa V_2 - V}$$

$$\begin{aligned} I_b &= e^{\kappa V_b} = I_1 + I_2 \\ &= I_0 e^{-V} \left( e^{\kappa V_1} + e^{\kappa V_2} \right) \end{aligned}$$

$$\Rightarrow e^V = \frac{e^{\kappa V_1} + e^{\kappa V_2}}{e^{\kappa V_b}}$$

# Differential Pair (III)

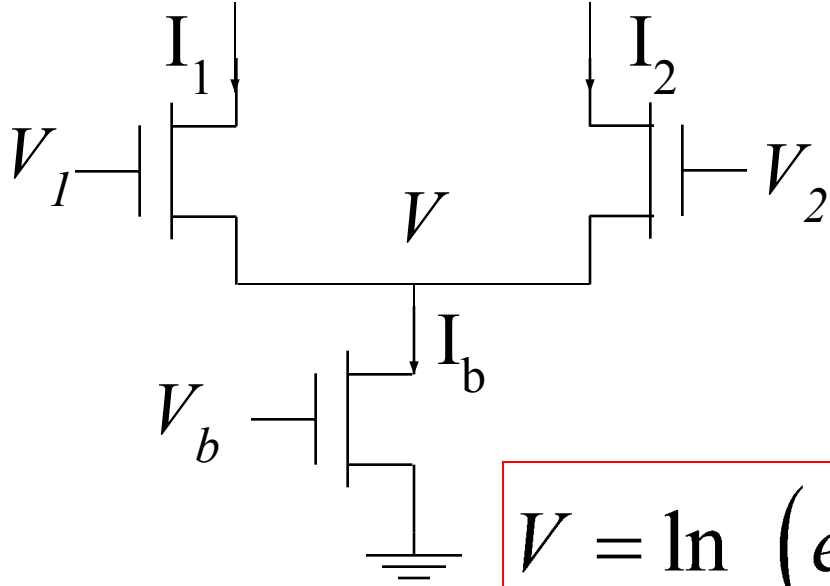

$$V = \ln \left( e^{\kappa V_1} + e^{\kappa V_2} \right) - \kappa V_b$$
$$\approx \kappa (V_1 - V_b) \text{ for } V_1 - V_2 \geq 100\text{mV}$$

# Differential Pair (IV)

Output currents:

$$I_1 = I_b \frac{e^{\kappa V_1/U_T}}{e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}} = \frac{I_b}{1 + e^{\kappa(V_2 - V_1)/U_T}}$$


$$I_2 = \frac{I_b}{1 + e^{\kappa(V_1 - V_2)/U_T}}$$

Fermi function

Difference of output currents:

$$I_1 - I_2 = I_b \frac{e^{\kappa V_1/U_T} - e^{\kappa V_2/U_T}}{e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}} = I_b \tanh \left( \kappa \frac{V_1 - V_2}{2U_T} \right)$$


## Differential Pair (IV)

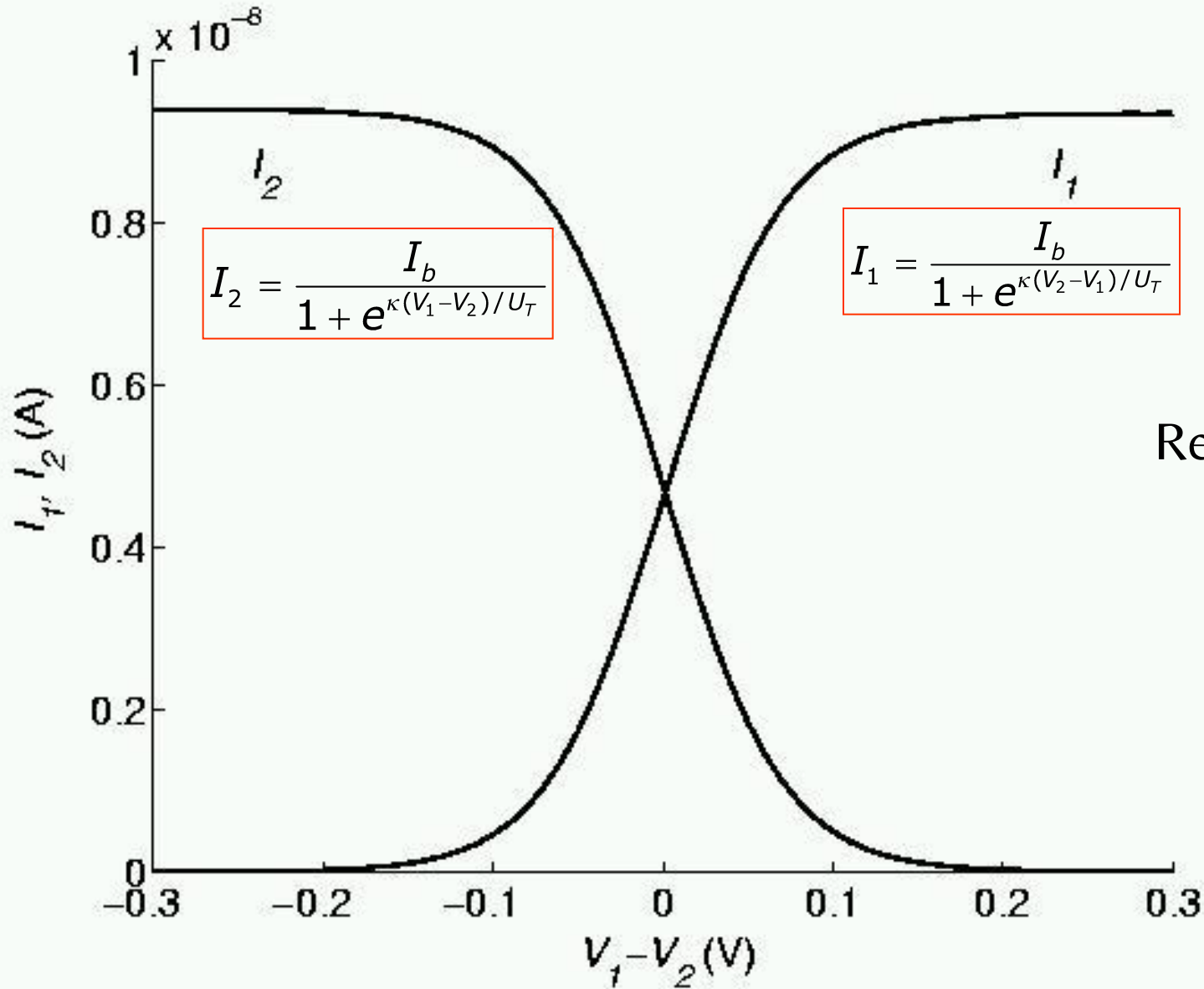

Remember sigmoid is

$$f(x) = \frac{1}{1 + e^{-\alpha x}}$$

# Output Current vs Differential Input

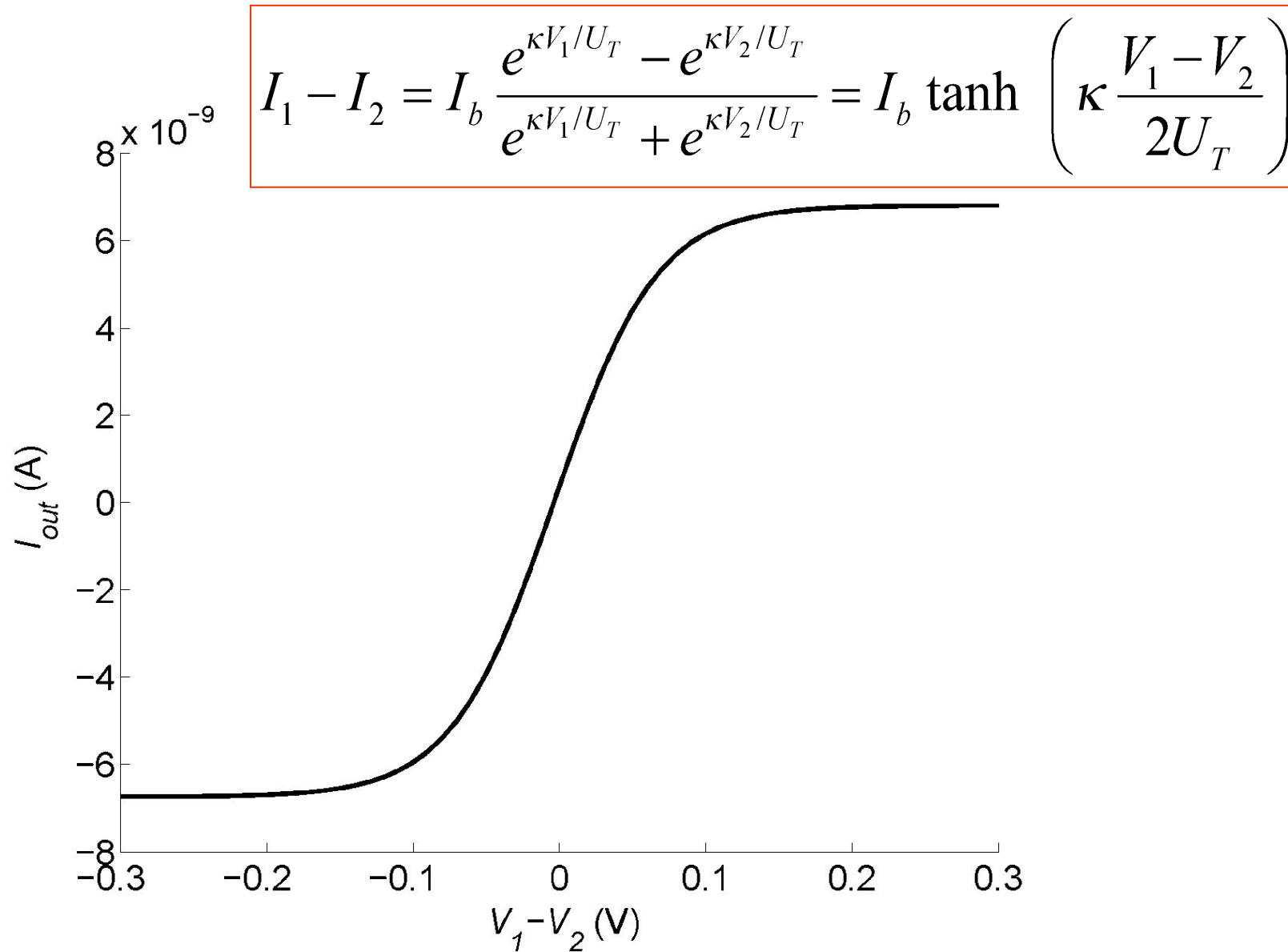




# Digression: Hyperbolic functions

$$\sinh(x) = \frac{e^x - e^{-x}}{2} \approx x \text{ for small } x$$


$$\cosh(x) = \frac{e^x + e^{-x}}{2} \approx 1 + \frac{x^2}{2} \text{ for small } x$$
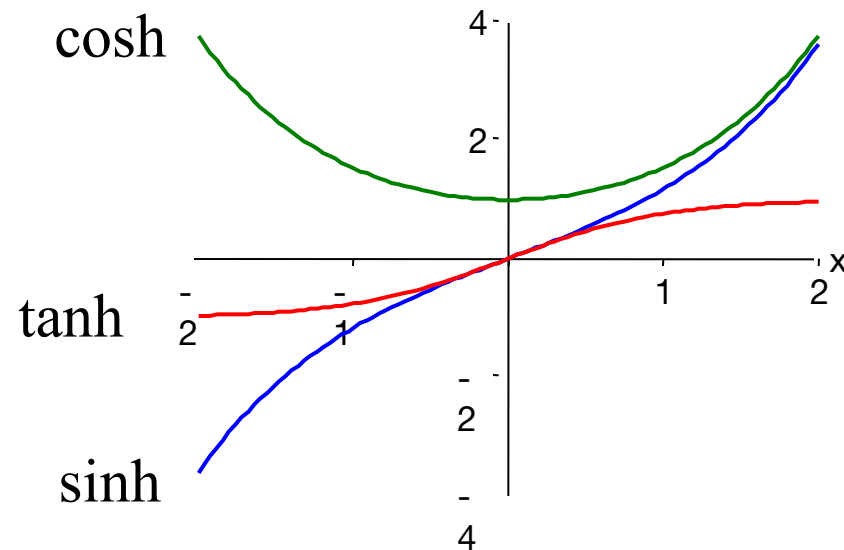
$$\tanh(x) = \frac{\sinh(x)}{\cosh(x)} = \frac{e^x - e^{-x}}{e^x + e^{-x}} \approx x \text{ for small } x$$



tanh: *compressive*  
sinh: *expansive*

# Transconductance Amplifier

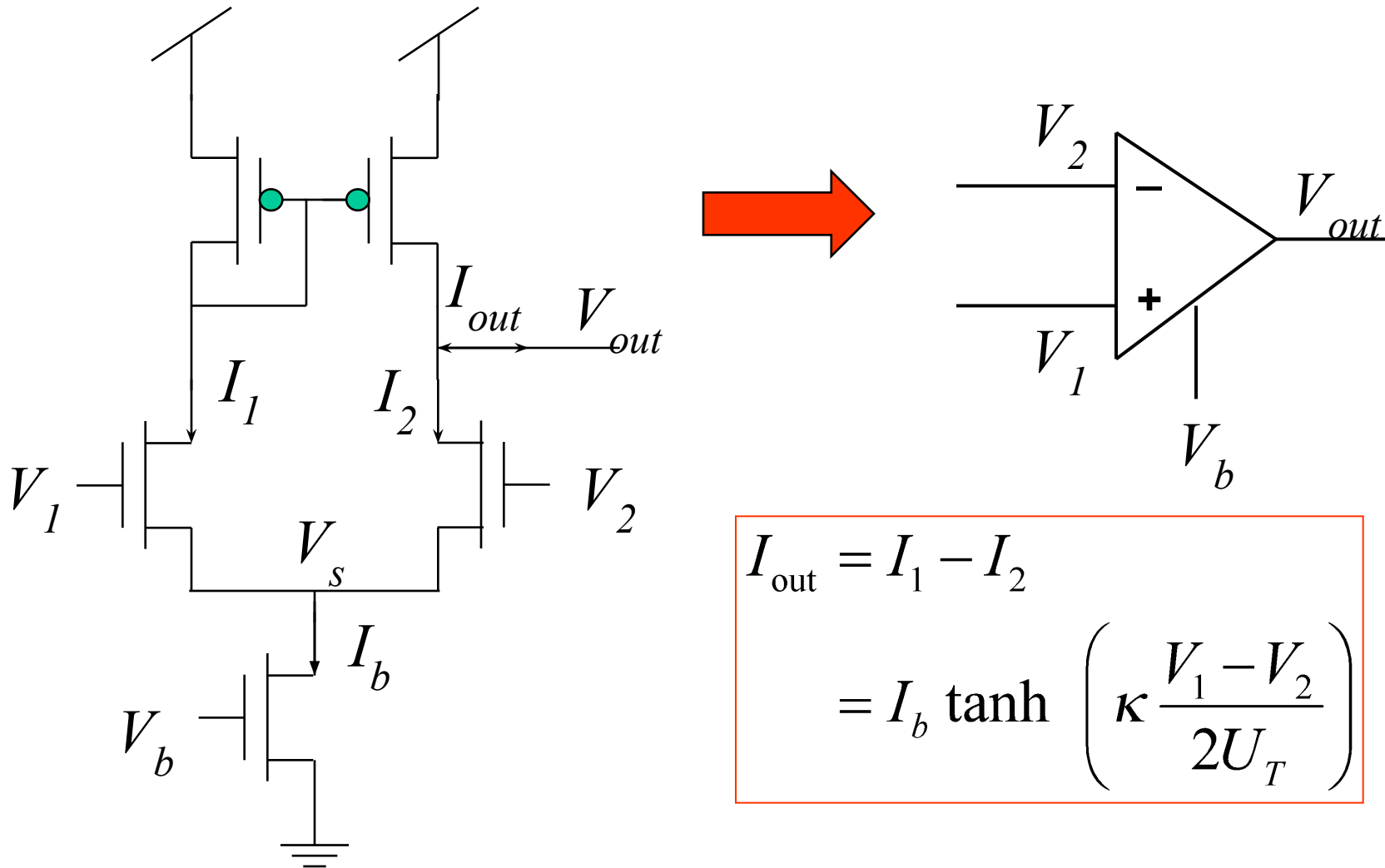

# Transconductance Amplifier

In subthreshold:

For small differential voltages ( $|V_1 - V_2|$  e.g.  $< 200\text{mV}$ ),  
the  $\tanh(\cdot)$  relationship is approximately linear :

$$I_{out} = I_b \tanh \left( \kappa \frac{V_1 - V_2}{2U_T} \right)$$

can be reduced to :

$$I_{out} \approx g_m (V_1 - V_2)$$

where

$$g_m \approx \frac{\kappa I_b}{2U_T}$$

# Transconductance Amplifier

Output conductance is defined as :

$$g_d = -\frac{\partial I_{out}}{\partial V_{out}} \approx \frac{I_b}{V_E}$$

# Transconductance in Strong Inversion

In above threshold, the output current of the diff pair is

$$I_1 - I_2 = \frac{\beta}{2}(V_1 - V_2) \sqrt{\frac{4I_b}{\beta} - (V_1 - V_2)^2}$$

where  $\beta = \mu C_{ox} \frac{W}{L}$ .

For  $|V_1 - V_2| = \sqrt{2I_b / \beta}$ , the transconductance is given by

$$g_m = \sqrt{\beta I_b}$$

# Differential pair in strong inversion (V)

• In **strong inversion**, solve for  $I_1$  &  $I_2$  this way:


$$\Delta V \equiv V_1 - V_2 = \sqrt{\frac{2I_1}{\beta}} - \sqrt{\frac{2I_2}{\beta}}$$

You eventually obtain


$$\text{for } \frac{\beta \Delta V^2}{2} < I_b \quad I_{1,2} = \frac{I_b}{2} \left( 1 \pm \sqrt{\frac{\beta \Delta V^2}{I_b} - \left( \frac{\beta \Delta V^2 / 2}{I_b} \right)^2} \right)$$

$$I_1 - I_2 = I_b \sqrt{\frac{\beta \Delta V^2}{I_b} - \left( \frac{\beta \Delta V^2 / 2}{I_b} \right)^2}$$
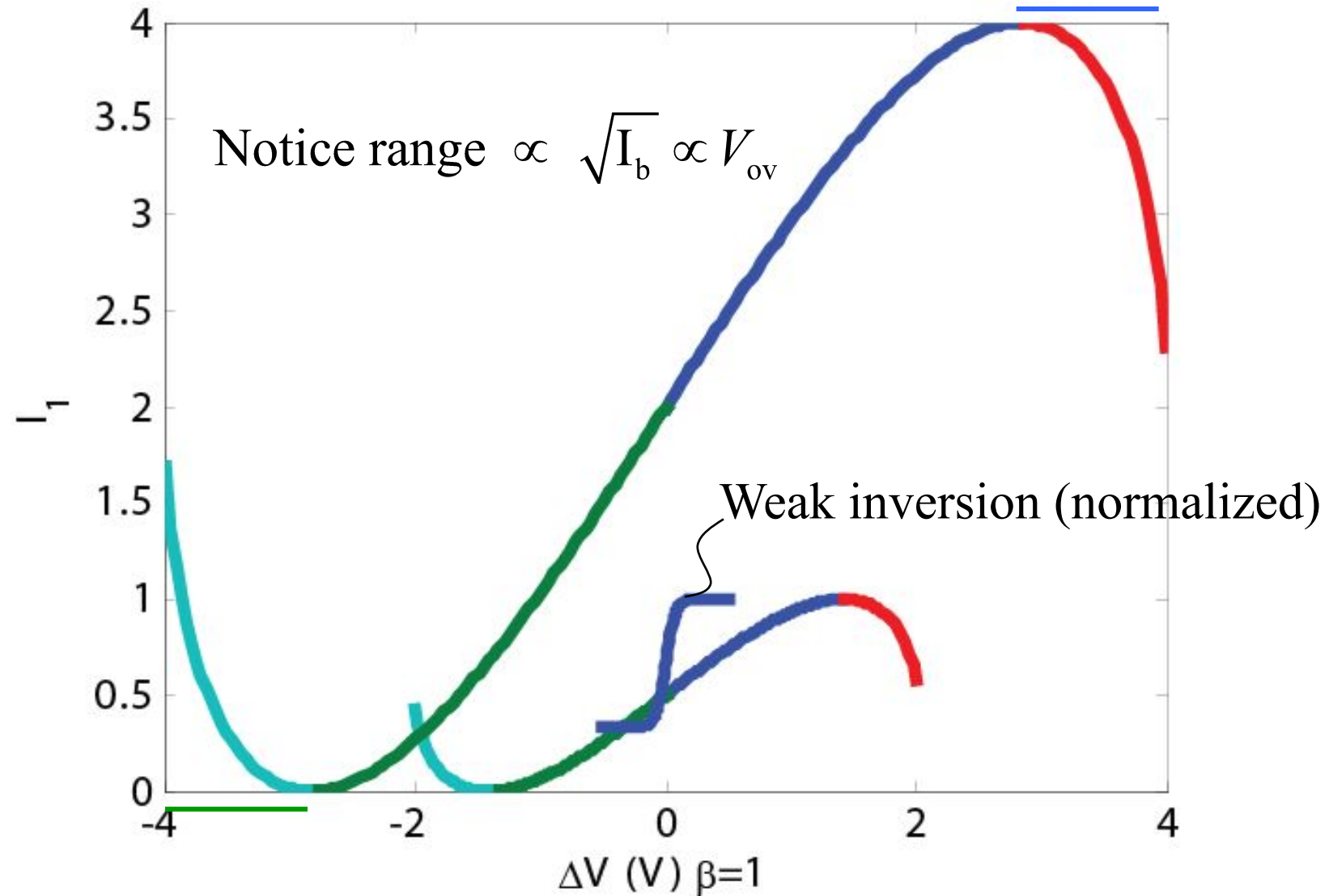
# Differential pair in weak and strong inversion



# Assumptions for Deriving Tanh Output

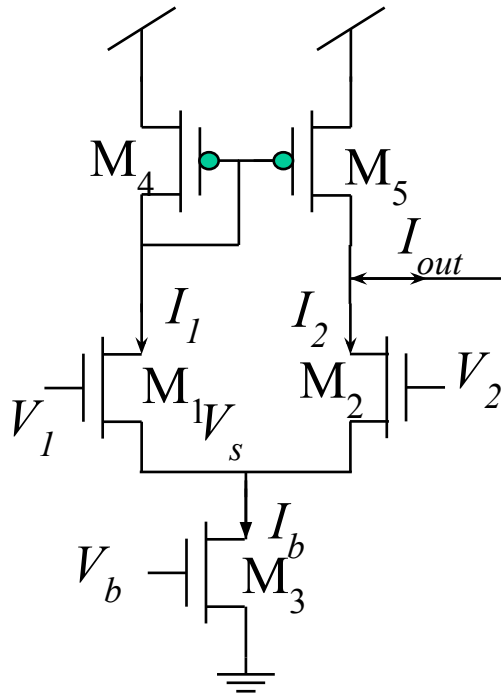

To obtain tanh function, we assume  $M_1$  to  $M_5$  are in saturation:

$$I_1 = I_0 e^{\kappa V_1 - V_s / U_T}$$

$$I_2 = I_0 e^{\kappa V_2 - V_s / U_T}$$

$$I_b = I_0 e^{\kappa V_b / U_T}$$

$$I_{out} = I_1 - I_2$$



# Deriving Common Source (I)

Assume bias transistor is not in saturation,

Equation for current through  $M_3$  is

$$I_b = I_0 e^{K V_b / U_T} \left( 1 - e^{-V_s / U_T} \right)$$


Assuming  $M_1$  and  $M_2$  are in saturation:

$$I_b = I_1 + I_2$$


$$e^{\kappa V_b/U_T} \left(1 - e^{-V_s/U_T}\right) = e^{(\kappa V_1 - V_s)/U_T} + e^{(\kappa V_2 - V_s)/U_T}$$

Solving for :
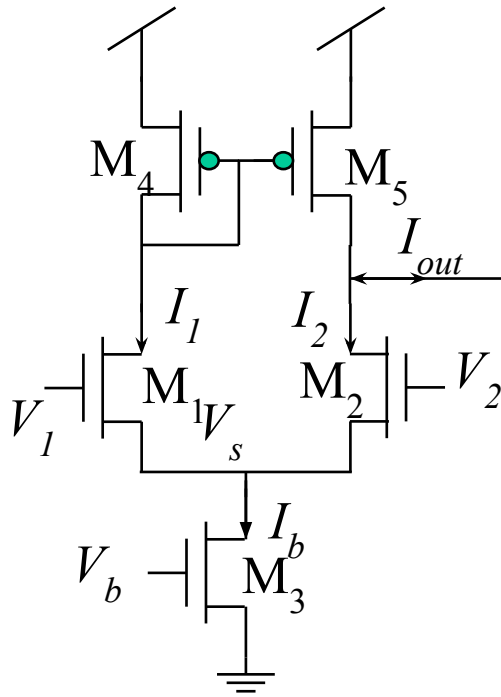
$$e^{-V_s/U_T} = \frac{e^{\kappa V_b/U_T}}{e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}} \quad (Eq.1)$$



# Deriving Common Source (II)

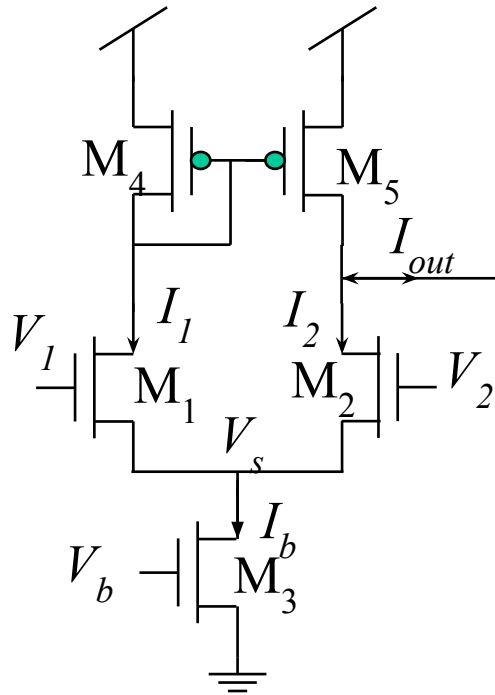


For the bias transistor to be in saturation,  
 $V_s > 4U_T$  therefore  $e^{-V_s/U_T} \ll 1$

$$e^{-V_s/U_T} = \frac{e^{\kappa V_b/U_T}}{e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}} \ll 1$$

$$e^{\kappa V_b/U_T} \ll e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}$$

$$\frac{e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}}{e^{\kappa V_b/U_T}} \gg 1 \quad (Eq.2)$$

# Deriving Common Source (III)

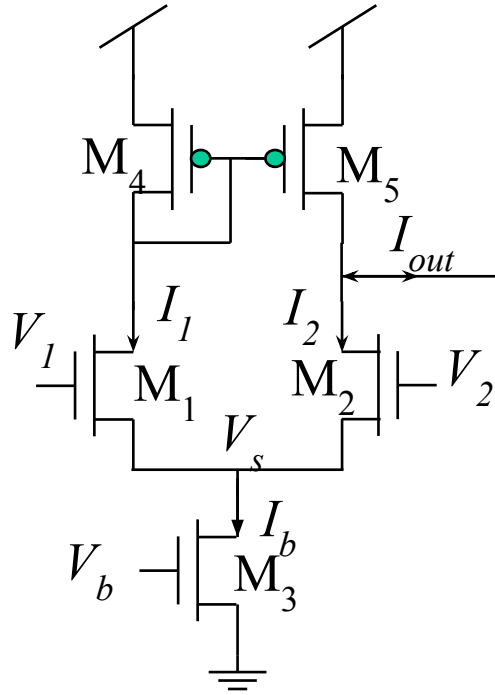

From

$$e^{-V_s/U_T} = \frac{e^{\kappa V_b/U_T}}{e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}}$$

we can derive:

$$V_s = -\kappa V_b + U_T \ln(e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T})$$

Since  $e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T} \gg e^{\kappa V_b/U_T}$  and assuming that  $|V_1 - V_2| > 4U_T$  we can simplify the  $\ln(\cdot)$ .

# Deriving Common Source (IV)

The common node voltage  $V_s$  of the transconductance amplifier is:


$$V_s = \kappa \left( \max(V_1, V_2) - V_b \right)$$

and the saturation condition for  $M_3$ ,  $V_s > 4U_T$  is :

$$\max(V_1, V_2) > V_b + \frac{4U_T}{\kappa}$$
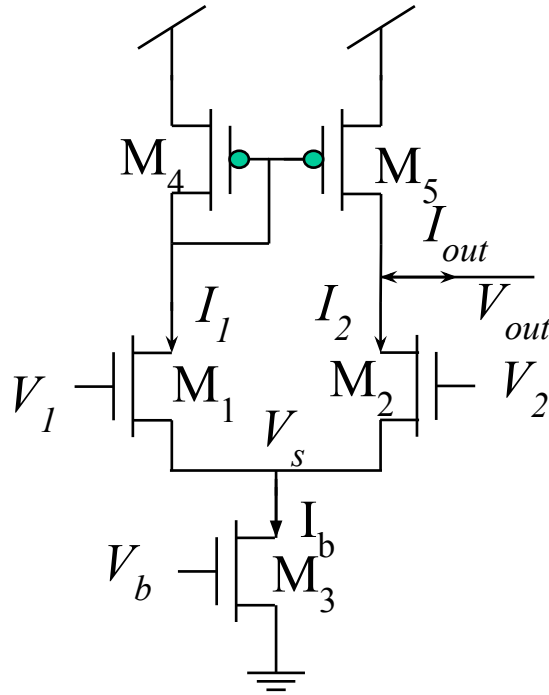
# Output Transistors

The output transistors  $M_2$  and  $M_5$  should also be in saturation:



To keep  $M_5$  in saturation :  $V_{dd} - V_{out} > 4U_T$

To keep  $M_2$  in saturation :  $V_{out} - V_s > 4U_T$

which means


$$V_{out} > \kappa (\max(V_1, V_2) - V_b) + 4U_T \quad (Eq.3)$$

Therefore there is a  $V_{min}$  problem, i.e. minimum  $V_{out}$  depends on  $V_1$ ,  $V_2$  and  $V_b$ .


Final condition :

$$\kappa (\max(V_1, V_2) - V_b) + 4U_T < V_{out} < V_{dd} - 4U_T$$

# Curves of $I_{out}$ vs $V_{out}$

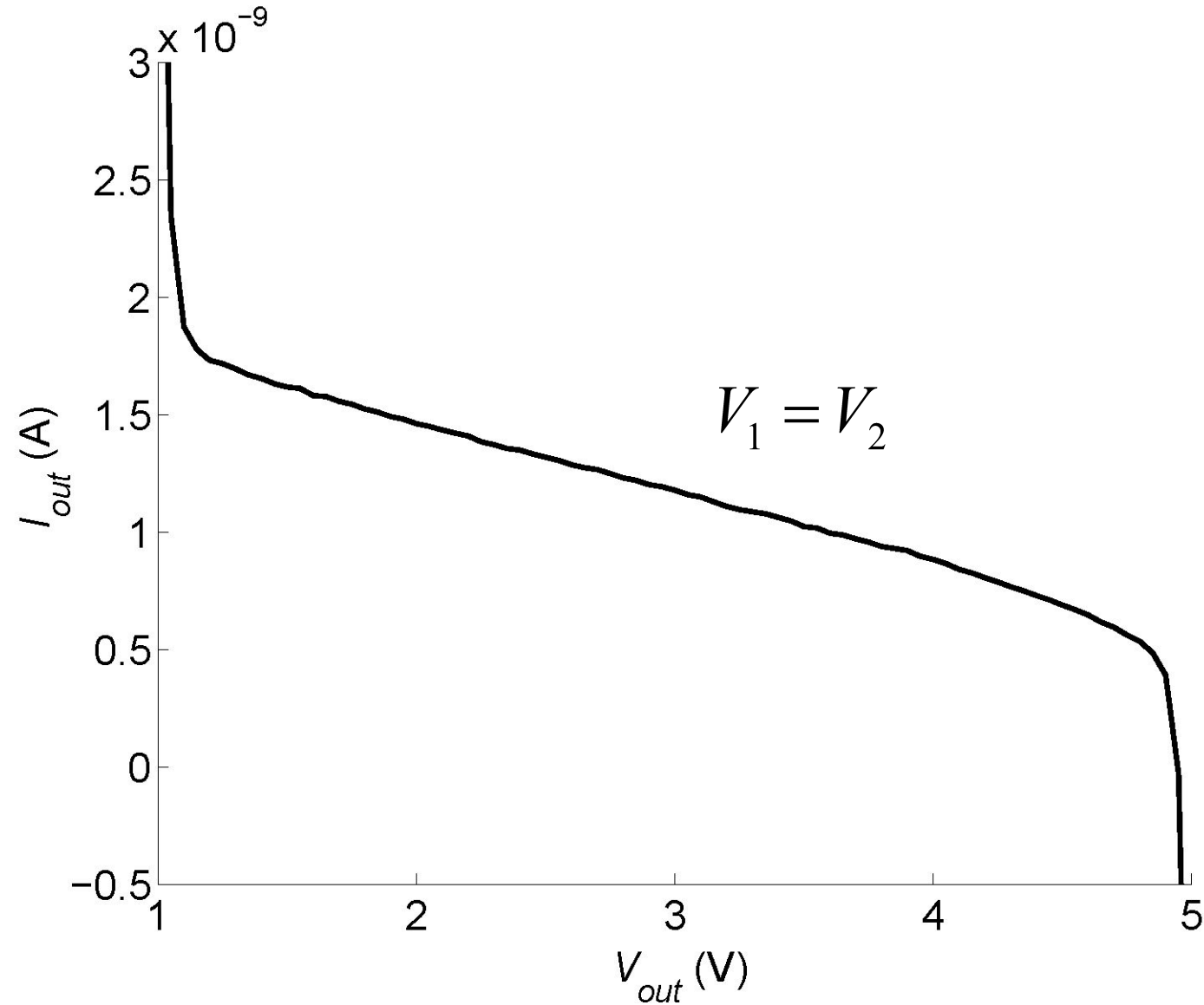

# Voltage Amplifier

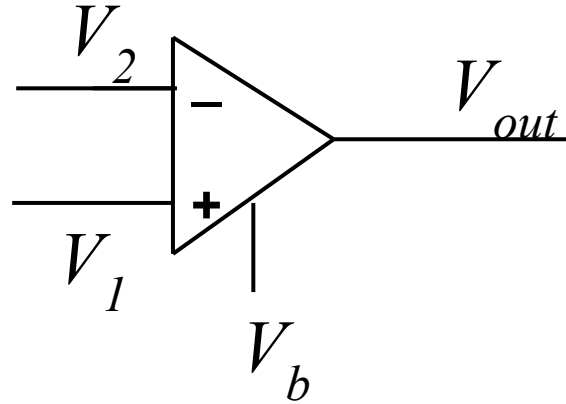

Transconductance amplifier can be used a differential-input voltage amplifier:

$$V_{out} = A(V_1 - V_2)$$

Transfer function :

$$A = \frac{dV_{out}}{d(V_1 - V_2)} = \frac{dI_{out}}{d(V_1 - V_2)} \frac{dV_{out}}{dI_{out}} = \frac{g_m}{g_d}$$


$$\text{Subthreshold : } A \approx \frac{\kappa V_E}{2U_T}; \text{ Above threshold : } A \approx \sqrt{\frac{\beta}{I_b}} V_E$$

# Voltage Amplifier

- The open-circuit voltage gain  $A$  increases with Early voltage, and therefore with the length of the output transistors.
- Typical subthreshold values are between 100 and 1000.
- Because of the large voltage gain and transistor mismatch effects, the amplifier is usually used in a negative-feedback configuration.
- In open-voltage mode, it is used mainly as a comparator.  $V_{out}$  is “high” when  $V_1 > V_2$  and vice-versa.



# Output Voltage Limits (I)

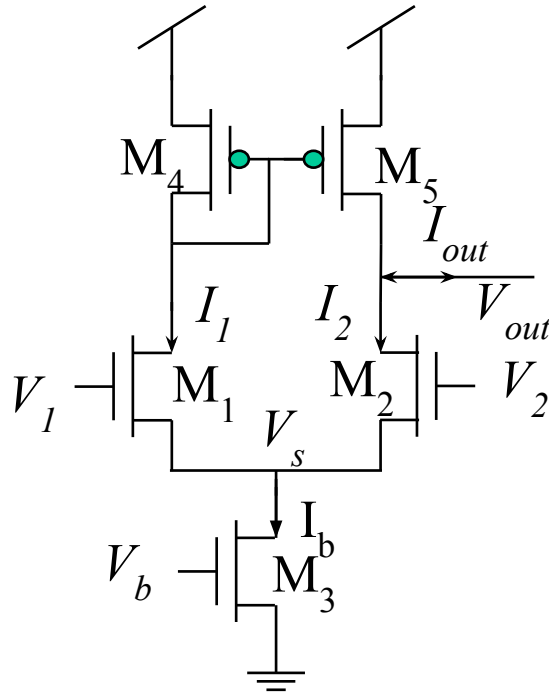

Compute limits of voltage swing

a)  $V_1 > V_2$

For  $V_1 > V_2 + 4U_T$  current through  $M_2$  is much smaller than  $M_1$ ,  $V_{out}$  goes almost to  $V_{dd}$  to shut off  $M_5$ .  $M_5$  goes out of saturation.

b)  $V_2 > V_1$

Forward current through  $M_2 \gg$  current through  $M_1$ .


Top current mirror forces  $I_1 \approx I_2$ .

If  $V_2 \gg V_1$ , voltage drop across  $M_2$  is close to 0,

$V_{out} = V_s$  and  $M_2$  goes out of saturation.
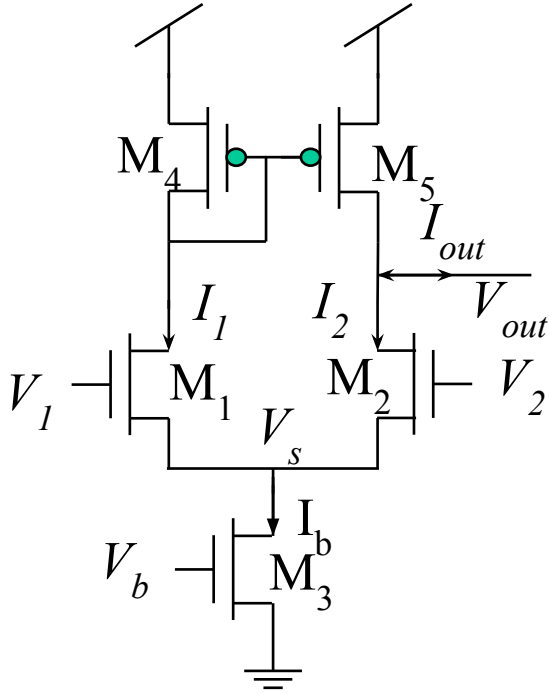
# Output Voltage Limits (II)

The output transistors  $M_2$  and  $M_5$  should also be in saturation:




Assume  $V_2 > V_1$  therefore  $V_{out} \approx V_s$

$$e^{-V_s/U_T} = \frac{e^{\kappa V_b/U_T}}{e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T} + e^{\kappa V_2/U_T}}$$

$$e^{-V_s/U_T} = \frac{e^{\kappa V_b/U_T}}{e^{\kappa V_b/U_T} + 2e^{\kappa V_1/U_T}}$$

$$e^{-V_s/U_T} = \frac{0.5e^{\kappa V_b/U_T}}{0.5e^{\kappa V_b/U_T} + e^{\kappa V_1/U_T}}$$

# Output Voltage Limits (III)

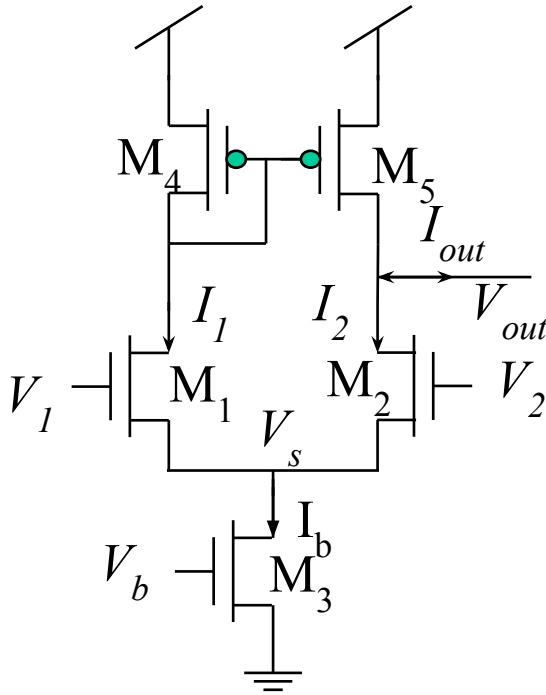

Assume  $V_2 > V_1$

a) If  $V_1 < V_b - (4 + \ln(2)) U_T / \kappa$

$$V_{out} \approx 0$$


b) If  $V_1 > V_b - (4 + \ln(2)) U_T / \kappa$

$$V_{out} \approx \kappa (V_1 - V_b) + U_T \ln(2)$$


Therefore,

$V_{out}$  increases linearly with  $V_1$  with a slope of  $\kappa$

# Output Voltage vs Input Voltage

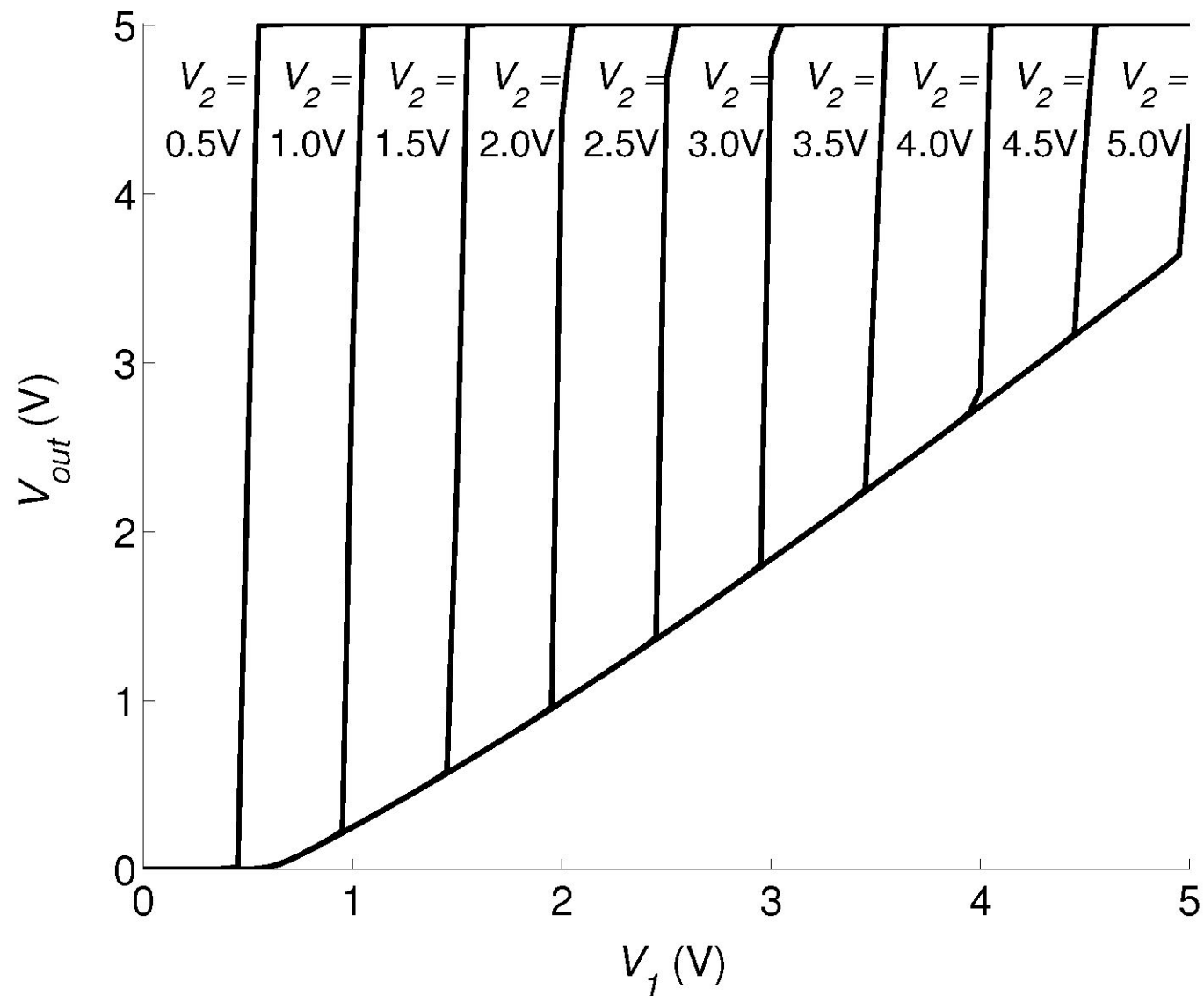

# Transconductance Amplifier

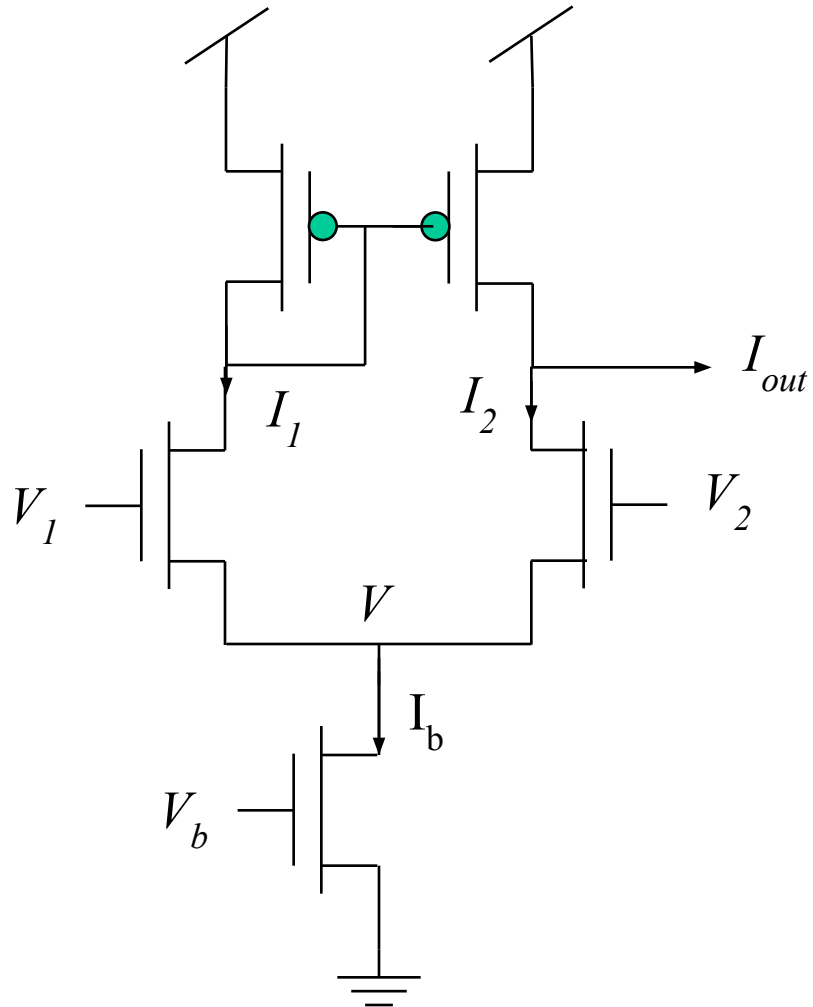


$$\begin{aligned} I_{out} &= I_1 - I_2 \\ &= I_b \tanh \left( \kappa \frac{V_1 - V_2}{2U_T} \right) \end{aligned}$$

Good: Simple, cheap

Bad: output voltage is restricted, voltage gain is limited
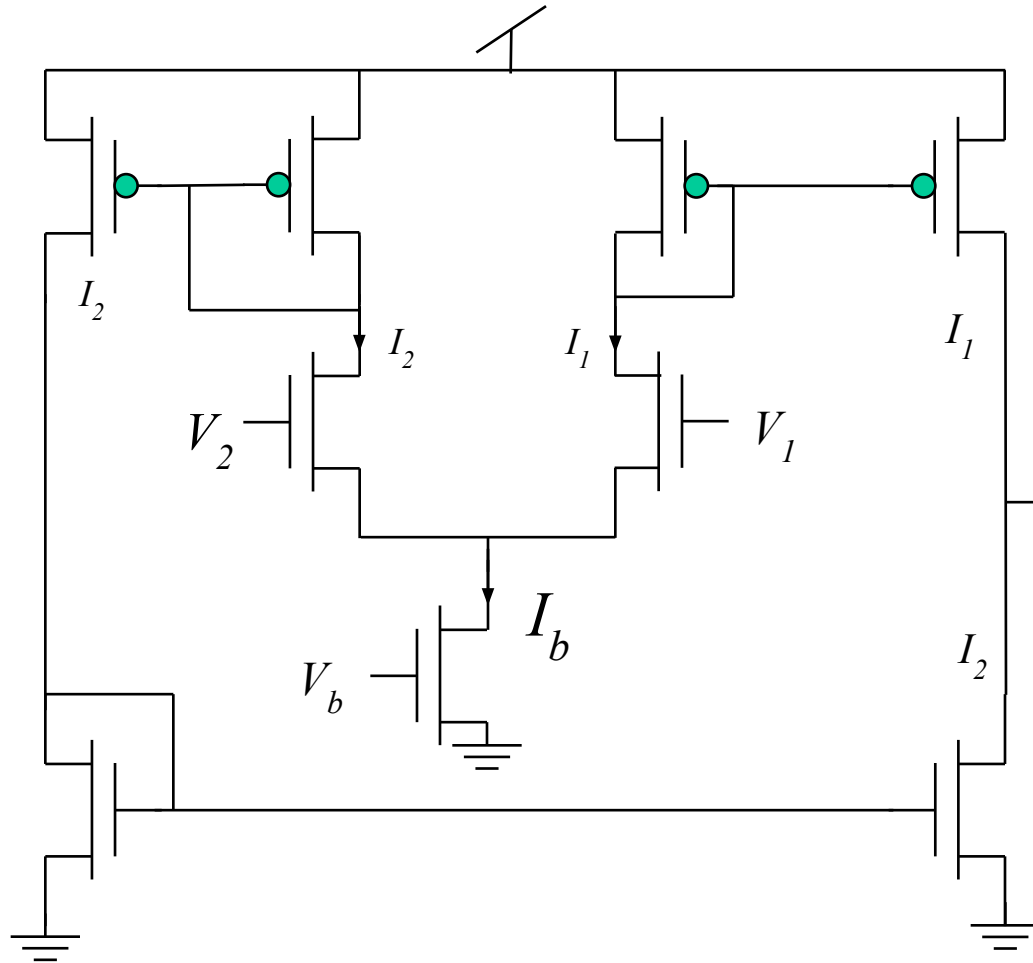
# Wide-Output Range Transconductance Amplifier



$$I_{out} = I_b \tanh \left( \kappa \frac{V_1 - V_2}{2U_T} \right)$$

Good: output voltage is unrestricted, gain can be  $>10^4$

Bad: larger, more mismatch

# THE END

Next week: Linear systems